

# Assignment on 4-bit MIPS Design, Simulation, and Implementation

1805006

Tanjeem Ajwad Zaman

1805016

Ahmed Hossain

1805019

MD Rownok Zahan Ratul

1805027

Nafis Karim

1805030

Md Toki Tahmid

August 2022

# 1 Introduction

This experiment focused on implementing a 4-bit microprocessor using both software and hardware. We utilized a 4-bit ALU and a 4-bit Data Bus. The address bus was 8 bits wide. We included 7 registers (6 mandatory - \$zero, \$t0, \$t1, \$t2, \$t3, \$t4 and 1 bonus register - \$sp for stack implementation). The control unit was microprogrammed: each operation had a corresponding control signal stored in a ROM. All instructions needed 1 clock cycle to be executed (and bonus push and pop pseudo-instructions needed 2-3 cycles). Thus the main components included a Program Counter, an Instruction Memory, a Register File, an ALU and a Data Memory. The data bus and address bus included MUXes, adders aside from wiring. Thus a reduced and modified version of the MIPS Instruction Set was implemented.

## 2 Given Instruction Set

Instruction ID	Instruction Type	Instruction
A	Arithmetic	add
B	Arithmetic	addi
C	Arithmetic	sub
D	Arithmetic	subi
E	Logic	and
F	Logic	andi
G	Logic	or
H	Logic	ori
I	Logic	sll
J	Logic	srl
K	Logic	nor
L	Memory	lw
M	Memory	sw
N	Control	beq
O	Control	bneq
P	Control	j

Figure 1: **Provided Instruction Set with Instruction Id's and Instruction Type.**

### 3 Assigned Instruction Serial

Instruction ID Serial	Instruction
E	and
K	nor
I	sll
M	sw
N	beq
H	ori
P	j
G	or
O	bneq
F	andi
L	lw
A	add
J	srl
D	subi
B	addi
C	sub

Table 1: Given Instruction Serial for Group 3

### 4 Control Unit Input and Outputs

	E	K	I	M	N	H	P	G	O	F	L	A	J	D	B	C
<b>ALU2</b>	0	1	1	0	0	0	x	0	0	0	0	0	1	0	0	0
<b>ALU1</b>	1	1	0	0	0	1	x	1	0	1	0	0	0	0	0	0
<b>ALU0</b>	0	0	0	0	1	1	x	1	1	0	0	0	1	1	0	1
<b>RegDst</b>	1	1	0	x	x	0	x	1	x	0	0	1	0	0	0	1
<b>Beq</b>	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
<b>MemRead</b>	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0
<b>MemWrite</b>	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
<b>MemtoReg</b>	0	0	0	x	x	0	x	0	x	0	1	0	0	0	0	0
<b>AluSrc</b>	0	0	1	1	0	1	x	0	0	1	1	0	1	1	1	0
<b>RegWrite</b>	1	1	1	0	0	1	0	1	0	1	1	1	1	1	1	1
<b>Jmp</b>	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
<b>Bne</b>	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0

Table 2: Control Unit Input Code and Corresponding Control Signal Outputs

## 5 Opcode For ALU

ALU Opcode	Action/Instruction
0000	Addition
0001	Subtraction
0010	And
0011	Or
0100	Shift Left
0101	Shift Right
0110	Nor
0111	Not Used

Table 3: ALU Opcode and Respective Action to Perform

## 6 Circuit Diagram

Complete circuit diagram of the 4 Bit MIPS is provided in the given subsections. It consists of 5 major modules:

1. Arithmetic Logic Unit (ALU)
2. Control Unit
3. Register File
4. Instruction Memory
5. Data Memory

### 6.1 Complete Circuit Diagram

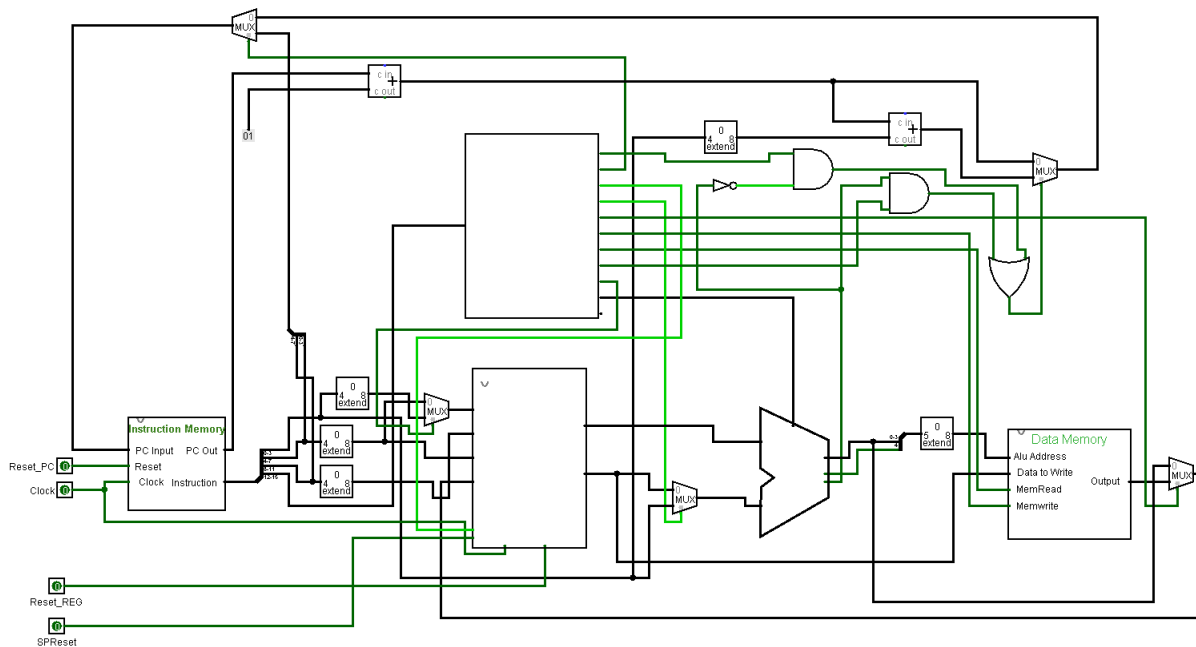


Figure 2: Complete Circuit Diagram with All Additional Components

## 6.2 Arithmetic Logic Unit (ALU)

 


Figure 3: Arithmetic Logic Unit(ALU)

## 6.3 Control Unit

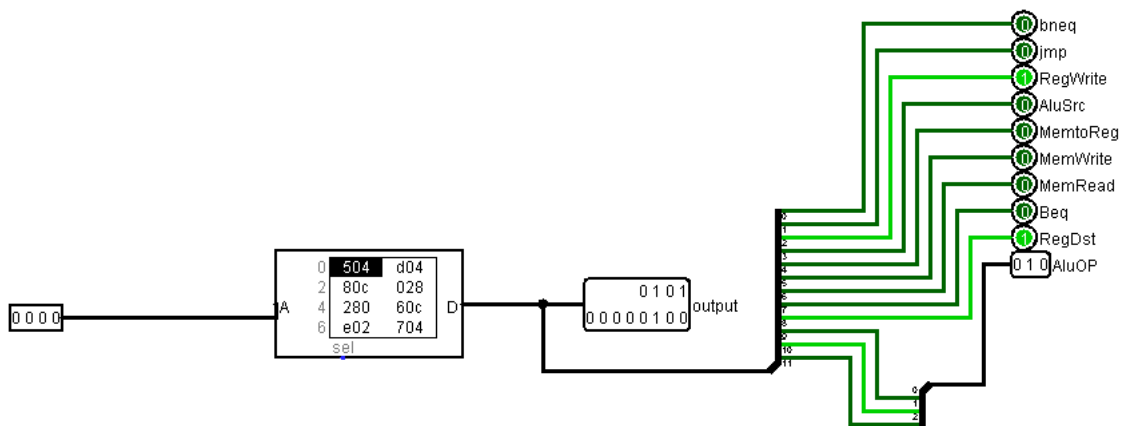


Figure 4: Control Unit for Providing Appropriate Control Signals on Given Opcode Input.

## 6.4 Register File

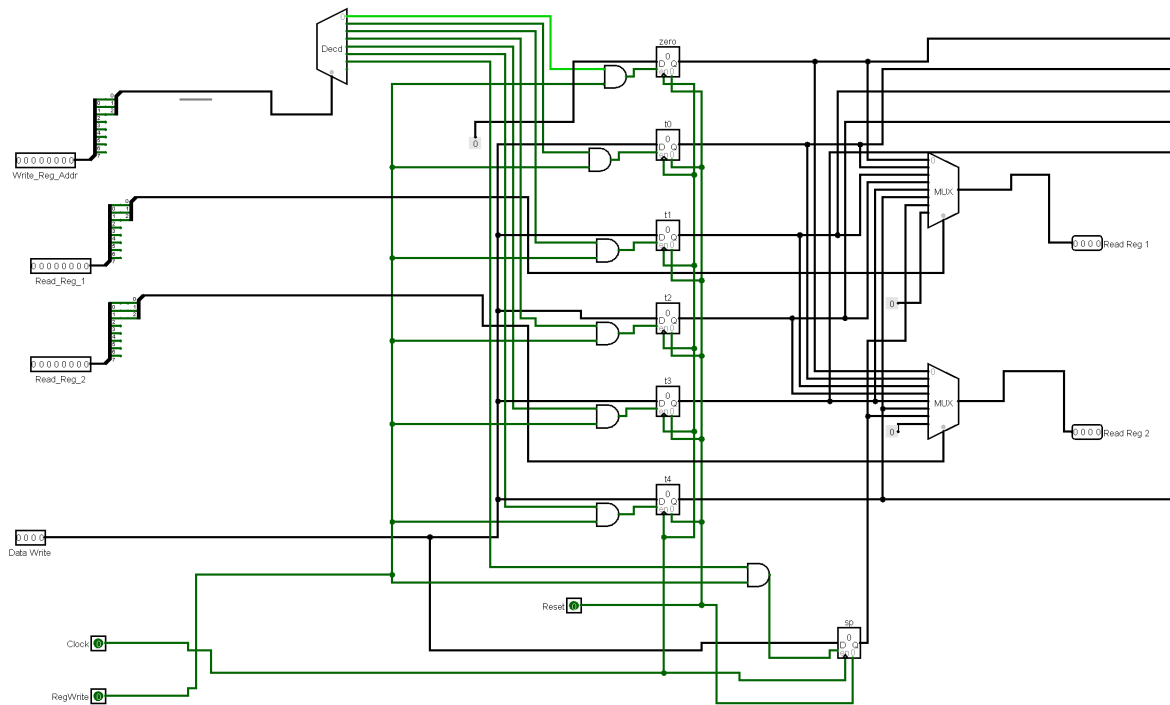


Figure 5: Register File Has 7 Registers(\$Zero,\$t0,\$t1,\$t2,\$t3,\$t4,\$t5, and \$sp) with 4 Data bits Output. The \$sp Register Is Used for Handling Push and Pop Instructions.

## 6.5 Instruction Memory

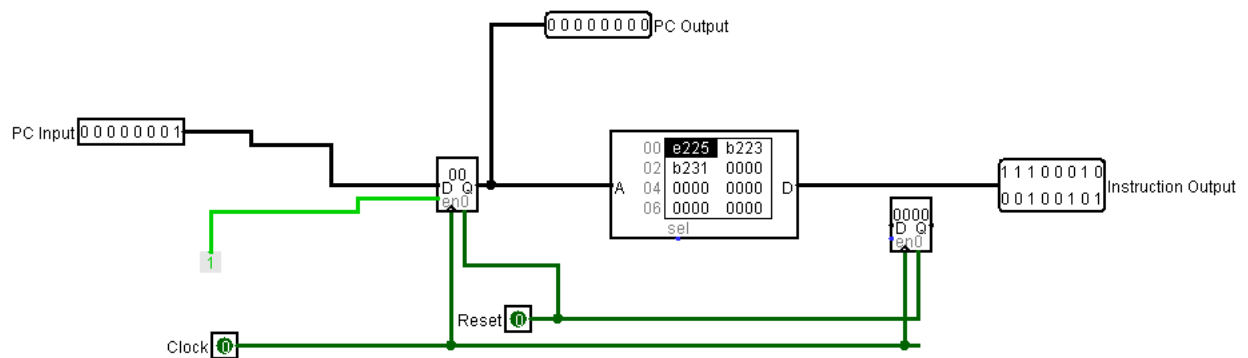


Figure 6: The Instruction Memory is Used to Load the Whole program into a ROM. The ROM has Address Bus of 8 Bits and Data Output Bus of 16 bits. Output of This Unit is a 16 bit Instruction According to the Given Instruction Format.

## 6.6 Data Memory

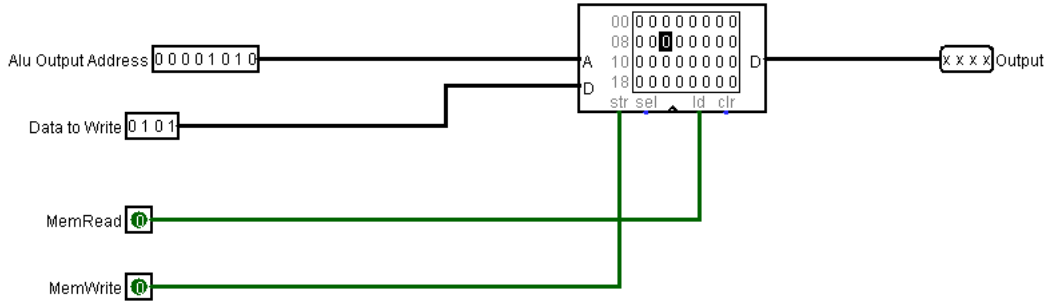


Figure 7: Data Memory Consists of a RAM That Serves to Load and Store Data into It. An Input Address Along with Data to be Written is Provided into the Data Memory. In Case of Load, a 4 Bit Data is Given as Output from the Data Memory

## 7 Gates Count

Gate Name	Count
And	10
Or	2
Not	2
Nor	2

Table 4: Used Logic Gates and Count

## 8 Discussion

- An instruction set similar to a miniature MIPS Instruction Set was implemented using a 4 bit micro-processor.
- Logisim was used for the software implementation.
- The hardware implementation used Atmega32 ICs for abstraction; ROMs (used in Instruction Memory, Control Unit), RAM (used in Data Memory), Register File, ALU.
- Seven registers (6 mandatory \$zero, \$t0, \$t1, \$t2, \$t3, \$t4 and one optional stack pointer \$sp) were implemented
- The corresponding MIPS-like code was parsed using a C++ program. The program generated the Machine Language code corresponding to our given specifications. This was loaded onto the IMs.
- **The PC register was operated on “rising-edge” and the Register File, Data Memory was operated on “falling edge”. Otherwise, some specific instruction sequences would create issues of unwanted writes.**
- The Stack was implemented from the top of Data Memory (0xFF). We added an extra command to set \$sp to 0xFF. This was done before starting operation.
- Push and Pop can be done by using the \$sp pointer accordingly.

*push \$t0*

was broken into 2 instructions :

*sw \$t0, 0(\$sp)*

*subi* \$sp,\$sp,1

similarly we expanded

*pop* \$t0

into 2 instructions :

*addi* \$sp,\$sp,1

*lw* \$t0,0(\$sp)

- Bit extensions were used for all addresses into Register file, since instructions had 4 bit addresses, but the address bus was 8 bits.