

Introduction:

An arithmetic logic unit (ALU) is a multi-operation, combinational logic digital function. It can perform a set of basic arithmetic operations. The ALU has a number of selection lines to select a particular operation in the unit. The selection lines are decoded within the ALU so that K selection variables can specify upto 2^K distinct operations.

We have three selection variables (cs) in our experiment which can enable us to perform $2^3 = 8$ distinct operations. The four data inputs from A are combined with the four inputs from B to generate an operation at the F outputs. The selection variable cs_2 distinguishes between arithmetic and logical operations while cs_1 is used as an input carry in our ALU design.


In our ALU design, we use a 4-bit status register. This status register contains 4 status bits that are denoted by C (Carry), S (Sign), V (Overflow) and Z (Zero). These status bits change during the arithmetic operations. They indicate the following changes:

- Carry flag (CF): Bit C is set when the output carry of the ALU is 1, otherwise it is 0.
- Sign flag (SF): Bit S is set when the highest order bit of the output of the ALU is 1, it is 0 when the highest order bit is 0.
- Overflow flag (OF): Bit V is set if the XOR of carries C_4 and C_5 is 1, otherwise it is 0.
- Zero flag (ZF): Bit Z is set if the result is 0, otherwise it is 0.

Problem specification:

Design a 4-bit ALU with three selection bits cs_2 , cs_1 and cs_0 for performing the following operations:

cs_2	$cs_1(Cin)$	cs_0	Functions
0	0	0	Subtract with borrow
0	0	1	Transfer A
0	1	0	Subtract
0	1	1	Increment A
1	X	0	AND
1	X	1	OR

 

Truth table and required k-maps:

1) Truth table for the functions:

S_2	$S_1(C_{in})$	S_0	F	X_i	Y_i	Z_i
0	0	0	$A-B-1$	A	B'	0
0	0	1	A	A	0	0
0	1	0	$A-1$	A	B'	1
0	1	1	$A+1$	A	0	1
1	X	0	AB	$A+B'$	B'	0
1	X	1	$A+B$	$A+B$	0	0

For the arithmetic operations, we take

S_1	S_0	Y_i	S_1	S_0	X_i
0	0	B_i'	0	0	A_i
0	1	0	0	1	A_i
1	0	B_i'	1	0	A_i
1	1	0	1	1	A_i

2) Truth table for determining X_i :

For the logical operations ($s_2=1$), we have,

s_2	s_1	s_0	X_i	Y_i	Z_i	Obtained F	Required F
1	0	0	A_i	B_i'	0	$A_i \oplus B_i'$	$A_i B_i'$
1	0	1	A_i	0	0	A_i	$A_i + B_i$
1	1	0	A_i	B_i'	0	$A_i \oplus B_i'$	$A_i B_i$
1	1	1	A_i	0	0	A_i	$A_i + B_i$

For $s_2 s_1 s_0 = 101$ and 111 , we require

$X_i = A_i + B_i$ so that,

$$X_i \oplus Y_i = A_i + B_i$$

for $s_2 s_1 s_0 = 100$ and 110 ,

$$A_i B_i = (A_i + P) \oplus B_i'$$

$$= (A_i + P)' B_i' + (A_i + P) B_i$$

$$= A_i' P' B_i' + A_i B_i + P B_i = A_i B_i + A_i B_i' P' + B_i P$$

For $P = B_i'$, we have $X_i \oplus Y_i = A_i B_i$.

\therefore We require $P = B_i'$ for $s_2 s_1 s_0 = 100$ and 110 .

3) Truth table for determining Y_i :

s_1	s_0	b_i	Y_i
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

K-map:

		$s_0 b_i$			
		00	01	11	10
s_1	0	1	0	0	0
	1	1	0	0	0

$$Y_i = s_0' b_i'$$

Combining the arithmetic and logical operations,

$$X_i = A_i + s_2 s_0' (A_i + B_i') + s_2 s_0 (A_i + B_i)$$

$$= A_i + A_i s_2 s_0' + A_i s_2 s_0 + B_i' s_2 s_0' + B_i s_2 s_0$$

$$= A_i (1 + s_2 s_0' + s_2 s_0) + B_i' s_2 s_0' + B_i s_2 s_0$$

$$= A_i + s_2 (B_i' s_0' + B_i s_0)$$

$$= A_i + s_2 (s_0 \odot B_i)$$

4) Truth table for determining Z_i :

s_2	s_1	s_0	Z_i
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

K-map:

		$s_1 s_0$			
s_2		00	01	11	10
	0	0	0	1	1
	1	0	0	0	0

$$z_i = s_2' s_1$$

Block diagrams:

 


Fig: Logic diagram of ALU

ii) Status register:

 


Fig: Block diagram of a status register.

Required ICs:

IC	Quantity

Discussion:

In this experiment, we were given the task to implement an ALU that can perform four arithmetic operations and two logical operations. We implemented the ALU in such a way that it can perform both arithmetic and logic operations in a single circuit, instead of requiring two different circuits. The number of ICs were kept as minimal as possible. Logisim - Win-2.7.1 simulation software was used to simulate the circuit.